



THE CATHOLIC UNIVERSITY OF EASTERN AFRICA

A. M. E. C. E. A

P.O. Box 62157

00200 Nairobi - KENYA

Telephone: 891601-6

Ext 1022/23/25

MAIN EXAMINATION

SEPTEMBER –DECEMBER 2021

FACULTY OF SCIENCE

DEPARTMENT OF NATURAL SCIENCES

REGULAR PROGRAMME

PHY 312: AC CIRCUIT THEORY

Date: DECEMBER 2021

Duration: 2 Hours


INSTRUCTIONS: Answer Question ONE and any TWO Questions

Q1.

- a) Giving mathematical expressions define Kirchhoff's laws ; **(3 marks)**
- b) An alternating voltage is given by $v = 282.8 \cos 314t$ volts. Find;
- i). the rms voltage, **(4 marks)**
 - ii). the frequency and **(3 marks)**
 - iii). the instantaneous value of voltage when $t = 4$ ms. **(3 marks)**
- c) A circuit consist of an inductor of 65mH and a capacitor of 20 μ F. Given that the circuit is at resonance, find the resonance frequency(f_0). **(4 marks)**
- d)
- i) What do you understand by the term resonance frequency in an R-LC circuit **(1 mark)**
 - ii) Show that the resonance frequency is given by $\omega_0 = \frac{1}{\sqrt{LC}}$. **(4 marks)**
- e) A 22 Ω resistor is connected to a battery of emf 3 V and an internal resistor of 1 Ω . Find;
- i) Total current in the circuit
 - ii) the terminal voltage of the battery
 - iii) the power delivered by the source voltage
 - iv) the power delivered to the external resistor **(8 marks)**


Q2.

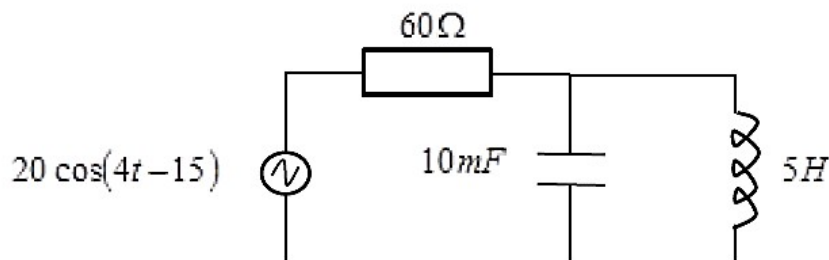- a) An ac voltage is given by the equation $V(t) = 36 \sin 3\pi t$. Determine;
 i). Phase constant **(6 Marks)**
 ii). Frequency of the ac voltage **(4 marks)**
- b)
- c) By expressing the source voltage in the circuit below in phasor form, determine the voltage across the 10mF capacitor. **(10marks)**



Q3.

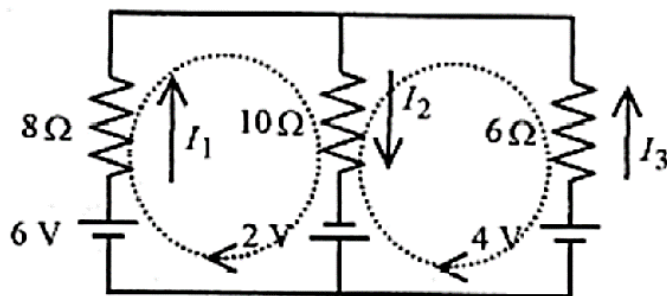- a) The circuit below represent a network of resistors with current I_1 , I_2 and I_3 flowing through the circuit as indicated. Taking advantage of the indicated loops. Solve for current I_1 , I_2 and I_3 using mesh current method. **(8 marks)**




- b) An AC voltage source with amplitude 15V and frequency 60Hz is applied across a 30mH inductor. Find the actual expression for the resulting AC current. **(6 marks)**
- c) An RLC circuit all connected in series with an emf source V . if the current flowing in the circuit is I , derive an expression for the total impedance Z of the circuit. **(6 marks)**

Q4.

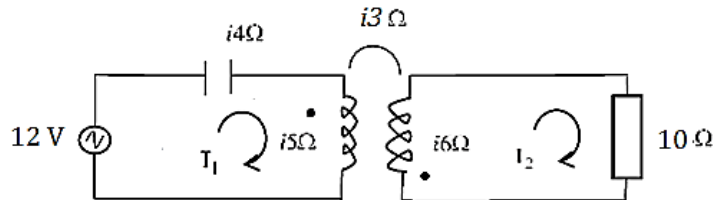- a) What do you understand by the terms; **(2 marks)**
 i). Mutual inductance


- ii). Magnetically coupled circuits
- b)
- Differentiate between instantaneous and average power giving mathematical expression in each case **(4 marks)**
 - State the dot convention principle in the two forms **(2 marks)**
- c) Calculate the phasor currents I_1 and I_2 in the circuit shown below **(6 marks)**




- d) Determine the capacitive reactance of a capacitor of $10\mu\text{F}$ when connected to a circuit of frequency **(6 marks)**
- 50 Hz
 - 20 kHz.

Q5.

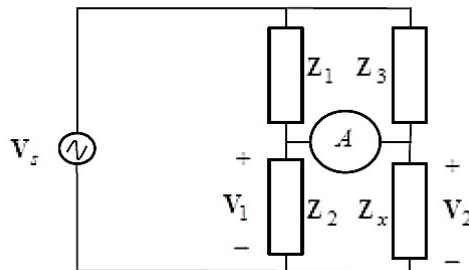- a) The ac bridge circuit in the figure below balances when Z_1 is a $1\text{k}\Omega$ resistor, Z_2 is a $4.2\text{k}\Omega$ resistor, Z_3 is a parallel combination of a $1.5\text{M}\Omega$ resistor and a 12pF capacitor, and $f = 2\text{ kHz}$. Find the series components that make-up Z_x . **(8 marks)**



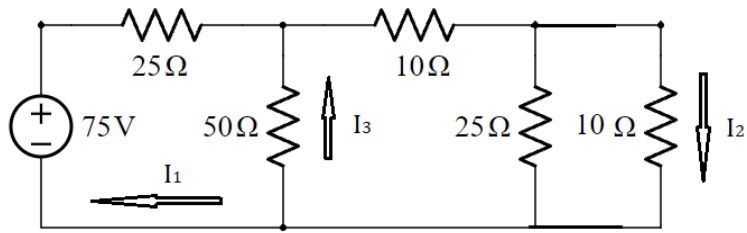- b) Considering that instantaneous power is given as $P(t) = V(t)I(t)$. Show that the time independent component of the instantaneous power is given as $\frac{1}{2}V_0I_0\cos(\Phi_v - \Phi_i)$. **(6marks)**
- c) Using node voltage method determine the current in the following circuit with reference to the indicated direction **(6 marks)**



DTE DEC 2021

END