



THE CATHOLIC UNIVERSITY OF EASTERN AFRICA

A. M. E. C. E. A

P.O. Box 62157

00200 Nairobi - KENYA

Telephone: 891601-6

MAIN EXAMINATION

MAY – JULY 2019 TRIMESTER

FACULTY OF SCIENCE

DEPARTMENT OF COMPUTER AND LIBRARY SCIENCE

SPECIAL / SUPPLEMENTARY EXAMINATION

CMT 201: LOGIC CIRCUITS

Date: JULY 2019

Duration: 2 Hours

INSTRUCTIONS: Answer Question ONE and any other TWO Questions

- Q1 a) Simplify: $(A \cdot B \cdot (C + \overline{B \cdot D}) + \overline{A \cdot B}) \cdot C \cdot D$ (4 marks)
- b) State the three notational methods for describing the behavior of gates and circuits (3 marks)
- c) State the three representations of an XOR gate (3 marks)
- d) Verify DeMorgan's law (3 marks)
- e) Draw a circuit diagram corresponding to the following Boolean expression;
 $(\overline{BC}) + (\overline{AB + C})$ (3 marks)
- f)
- g) Consider the K-map shown in Figure 1.

	00	01	11	10
	0	0	1	0
	1	1	0	1

Figure 1

State, in short hand notation, the

- (i) Minterm (3 marks)
- (ii) Maxterm (3 marks)
- h) Convert
- (i) decimal number 853 to Excess-3 (1 mark)
- (ii) 7CH to its octal equivalent (1 mark)
- (iii) decimal number 59.72 to its BCD (1 mark)
- (iv) hexadecimal number 14B16 to its binary equivalent (1 mark)
- Q2 i) If $(10n01)_2 = (33)_r$. Find both n and r . (4 marks)
- a) Consider the function: $Y = AB + (\overline{A}C) \cdot \overline{B}$
- (i) Draw a combinational logic circuit that implements this function. (3 marks)
- (ii) Draw a truth table for this function (3 marks)
- (iii) Write a sum-of-products representation of Y (2 marks)
- (iv) Write a product-of-sums representation of Y (2 marks)
- b) A combinational circuit has 3 inputs A, B, C and output F.
- F is true for following input combinations:
- A is False, B is True.
- A is False, C is True.
- A, B, C are False.
- A, B, C are True.
- Use the convention True=1 and False = 0
- (i) draw the Truth table for F (4 marks)
- (ii) Write the simplified expression for F in SOP form using Karnaugh map. (6 marks)
- Q3 a) Simplify the following Boolean expressions using a Karnaugh map. `
- $(A, B, C, D) = (C + D') + \overline{A}C\overline{D} + A\overline{B}C + \overline{A}\overline{B}C\overline{D} + ACD$
- (8 marks)
- b) Using minterms, show that
- $\overline{a} \cdot c + \overline{b} \cdot \overline{c} + a \cdot b = \overline{a} \cdot \overline{b} + b \cdot c + a \cdot \overline{c}$ (5 marks)

- c) Design a combinational logic circuit that converts 4 bits binary to gray code
(7 marks)

- Q4 a) Determine the number of gates required to minimize the Boolean function $Y = AB + CD$ using only 2 input NAND gates (6 marks)

- b) Simplify the Boolean expression using Boolean laws hence verify using a truth table

$$f(w, x, y) = w\bar{x}y + wx + w\bar{y} + wx\bar{y} \quad (7 \text{ marks})$$

- c) Design a combinational logic circuit (include block diagram and truth table) that performs arithmetic operation for adding three bits? (7 marks)

- Q5 a) Draw a circuit that will satisfy the following conditions; A combinational feedback paths, one input x and one output z , 2 secondary variables y_1 and y_2 and 2 excitation variables Y_1, Y_2 such that the logic equations for the excitation variables in terms of the circuit input and secondary variables are

$$Y_1 = xy_1 + \bar{x}y_2, Y_2 = x\bar{y}_1 + \bar{x}y_2 \quad \text{and that } Z = \bar{Y}_1.Y_2 \quad (10$$

marks).

- b) Design a combinational logic circuit that compares two, 2 bits binary numbers X and Y (10 marks)

END