

THE CATHOLIC UNIVERSITY OF EASTERN AFRICA

A. M. E. C. E. A

P.O. Box 62157

00200 Nairobi - KENYA

MAIN EXAMINATION

Telephone: 891601-6

Ext 1022/23/25

SEPTEMBER –DECEMBER 2021

FACULTY OF SCIENCE

DEPARTMENT OF NATURAL SCIENCES

REGULAR PROGRAMME

PHY 407: ELECTRONIC MEASUREMENT AND INSTRUMENTATION

Date: DECEMBER 2021 Duration: 2 Hours

INSTRUCTIONS: Answer Question ONE and any TWO Questions

Q1.

- a) Define the following with reference to measurement;
 - i). Unit
 - ii). Fundamental units
 - iii). Derived units

(3 marks)

b) Differentiate between analog and digital instrument

(2 marks)

c) A voltage has a true value of 1.50 V. An analog indicating instrument with a scale range of 0-2.50 V shows a voltage of 1.46 V. What is the value of absolute error?

(2 marks)

- d) State any three electrical physical quantities indicating the unit for each physical quantity (6 marks)
- e) An instrument records temperature of a body as 68°F. What value would another instrument calibrated in Kelvin give for the same temperature.

(3 marks)

f) List any two elements of an electronic device

(2 marks)

g) Describe any three systems for mechanical units

(6 marks)

h) What is dimension?

- (1 mark)
- i) With reference to dimension of charge and work done, show that the dimension for resistance is given as $ML^2T^{-3}I^{-2}$ (4 marks)
- j) A digital voltmeter has a read-out reading from 0 to 9,999 counts. Determine the resolution of the instrument in volt when the full scale reading is 9.999 V.

Q2.

a) Describe the term error as used in instruments

(2 marks)

b) Explain any four sources of errors in measurement

(8 marks)

- c) The expected value of the voltage across a resistor is 80 V. However, the measurement gives a value of 79 V. Calculate the; (10 marks)
 - i). absolute error,
 - ii). % error,
 - iii). relative accuracy, and
 - iv). % of accuracy.

Q3.

a) Define the following terms as applied in measurement:


(3 marks)

- i). Accuracy
- ii). Precision
- iii). Resolution
- b) Explain dynamic characteristics of instruments in detail

(10 marks)

c) The figure below shows a D.C ammeter. Considering that the source current is I, show that the shunt resistance is given by; (4 marks)


$$R_{sh} = \frac{I_m R_m}{I - I_m}$$

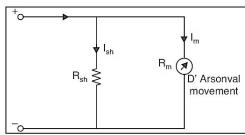

d) A 1 mA meter movement with an internal resistance of 100 W is to be converted into 0–100 mA. Calculate the value of shunt resistance required (3 marks)

Q4.

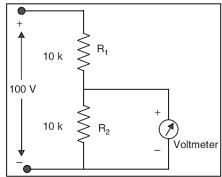a) Figure below shows a simple series circuit of R₁ and R₂ connected to a 100 V dc source.



If the voltage across R₂ is to be measured by voltmeter having

- i). A sensitivity of 1000 W/V, and
- ii). A sensitivity of 20,000 W/V,

Find which voltmeter will read the accurate value of voltage across R2. Both meters are used on the 50 V range. (10 marks)

- b) A 50 W basic movement requiring a full scale current of 1 mA is to be used as series ohmmeter. The internal battery voltage is 3 V. A half scale deflection marking desired is 1000Ω . Calculate (10 marks)
 - i). Values of R_{se} and R_{sh}
 - ii). Maximum value of R_{sh} to compensate for a 5 % drop in battery voltage

Q5.


a) Describe the three classes of resistors

(3 marks)

b) In a measurement of resistance by potentiometer, the voltage drops across a resistor under test and across 0.025 Ω standard resistors were found to be 0.882 V and 1.2 V respectively. Determine the value of resistor under test.

(4 marks)

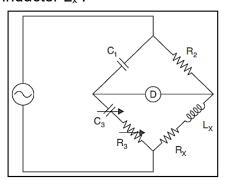c) The figure below shows a bridge for measuring self inductance of an unknown inductor $L_{\rm x}$.



Show that the unknown inductance is given as;

(5 marks)

$$L_x = R_2 R_2 C_1$$

d) With the aid of a well labelled diagram, discuss briefly, the basic parts of cathode ray oscilloscope (8 marks)



END